

**Rajmani Kumar,**  
**Lecturer, Dept. of BCA**  
**S.U.College, Hilsa (Nalanda)**  
**Patliputra University, Patna**

BCA-2<sup>nd</sup> Year

Paper-III

## Functions of Combinational Logic(Adder)

### Adder

An adder is a kind of calculator that is used to add two binary numbers. When I say, calculator, I don't mean one with buttons, this one is a circuit that can be integrated with many other circuits for a wide range of applications. There are two kinds of adders;

1. Half adder
2. Full adder

### 1.Half Adder

The half adder takes two single bit binary numbers and produces a sum and a carry-out, called "carry".

Here is the truth table description of a half adder. We denote the sum  $A + B$ .

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Written as a standard sum, the last row represents the following:

$$\begin{array}{r} 01 \\ +01 \\ \hline 10 \end{array}$$

The sum column indicates the number to be written in the unit's column, immediately below the two 1's. We write a 0 and carry a 1.

## The Half Adder and the Full Adder

In all arithmetics, including binary and decimal, the half adder represents what we do for the unit's column when we add integers.

There is no possibility of a carry-in for the unit's column, so we do not design for such. Another way is to say that there is a carry-in; it is always 0.

The full adder in decimal arithmetic would be used for the other columns: the ten's column, the hundred's column, and so on.

For these columns, a non-zero carry-in is a distinct possibility

Considered this way, we might write our sums table as follows.

$$2 + 2 = 4, \text{ if the carry-in is } 0, \text{ and}$$

$$2 + 2 = 5, \text{ when the carry-in is } 1.$$

Admittedly, the complexities of decimal arithmetic suggest another way, just add the values as three numbers, here  $2 + 2 + 1 = 5$ .

### Implementing the Half Adder

Here again is the truth table for the half adder.

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

We need equations for each of the Sum and Carry. Because we have used a truth table to specify these functions, we consider Boolean expressions.

Note that the carry is the logical AND of the two inputs:  $\text{Carry} = \mathbf{A \cdot B}$

The sum can be given in two equivalent expressions. The simplest expression uses the exclusive OR function:


$$\text{Sum} = \mathbf{A \oplus B}$$

An equivalent expression in terms of the basic AND, OR, and NOT is:

$$\text{Sum} = \overline{A} \cdot B + A \cdot \overline{B}$$
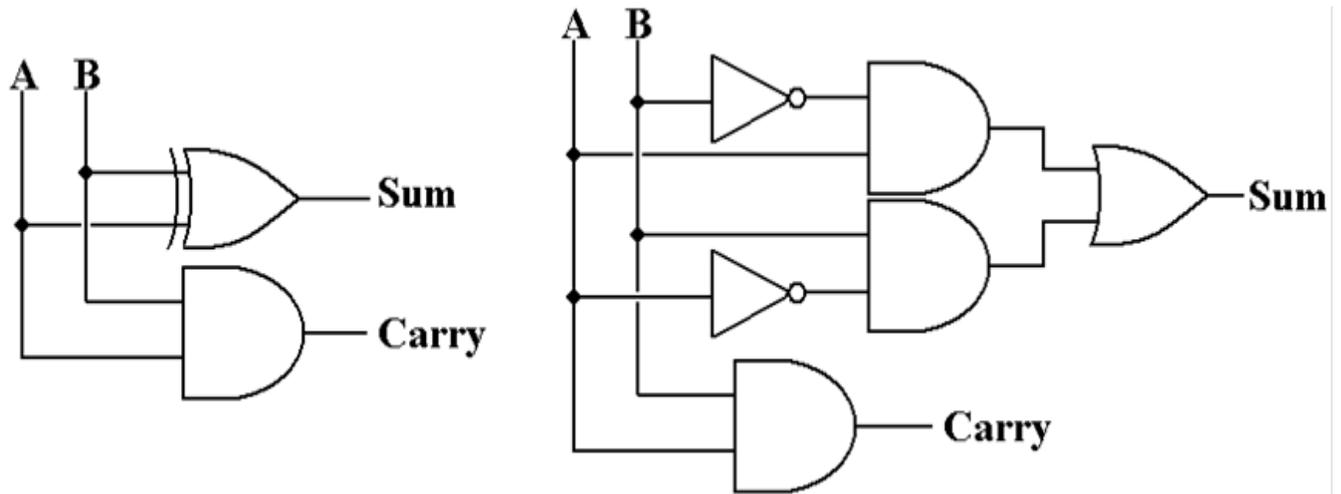
### Circuits for the Half Adder

Here are two slightly different circuit implementations of the half adder.



The circuit on the left implements the sum function as  $\text{Sum} = A + B$

The circuit on the right implements the sum function as

$$\text{Sum} = \overline{A} \cdot B + A \cdot \overline{B}$$

### Implementing the Full Adder

Here we show the truth table for the sum of A and B, with carry-in of C.

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


To read this as decimal, pretend that the Sum is “Sum\_Bit” and read as the Decimal\_Sum = Carry 2 + Sum\_Bit.

$$\text{So } 1 + 1 + 0 = 1 \times 2 + 0 = 2 \text{ (decimal), and}$$

$$1 + 1 + 1 = 1 \times 2 + 1 = 3 \text{ (decimal).}$$
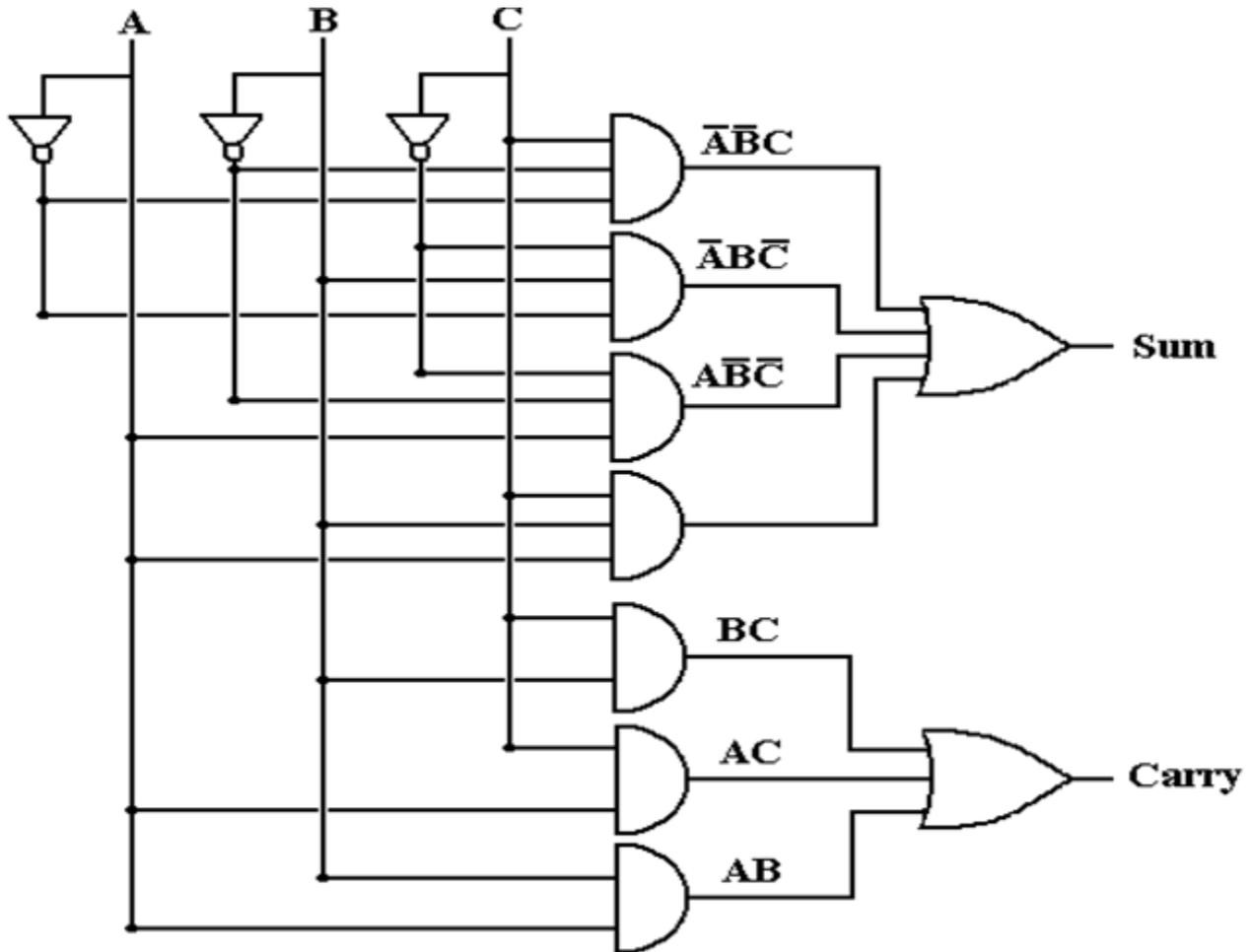
### One Circuit for the Full Adder

Here is the traditional AND/OR/NOT circuitry for the full adder.



### **The Full Adder with C = 0**

The circuit above implements the following two expressions, where C is the carry-in to the full adder.

$$\text{Sum} = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C$$

$$\text{Carry} = A.B + A.C + B.C$$

Suppose we let the carry-in  $C = 0$ . Then  $\bar{C} = 1$ .

What we have then is as follows.

$$\begin{aligned} \text{Sum} &= \bar{A}.\bar{B}.0 + \bar{A}.B.1 + A.\bar{B}.1 + A.B.0 \\ &= \bar{A}.B + A.\bar{B} \end{aligned}$$


$$\begin{aligned} \text{Carry} &= A.B + A.0 + B.0 \\ &= A.B \end{aligned}$$

As expected, a full adder with carry-in set to zero acts like a half adder.
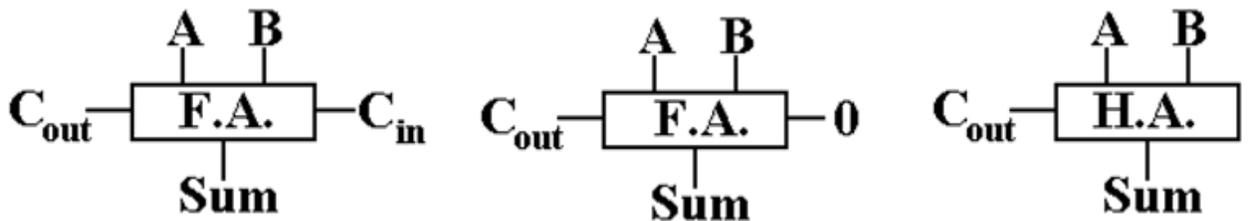
### The Full-Adder and Half-Adder as Circuit Elements

When we build circuits with full adders or half adders, it is important to focus on the functionality and not on the implementation details.

For this reason, we denote each circuit as a simple box with inputs and outputs.




The figure on the left depicts a full-adder with carry-in as an input.

The figure on the right depicts a half-adder with no carry-in as input.

The figure in the middle depicts a full-adder acting as a half-adder.
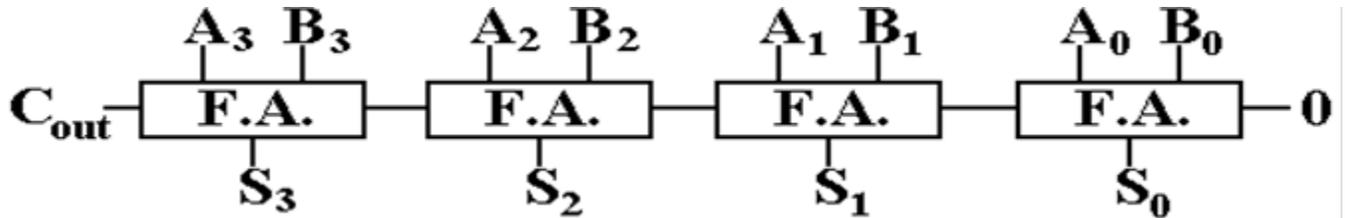
## A Four-Bit Full-Adder

Here is a depiction of a four-bit full adder to add two binary numbers, depicted as  $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$ .



Note that the carry-out from the unit's stage is carried into the two's stage. In general, the carry is propagated from right to left, in the same manner as we see in manual decimal addition. This is called a **“ripple carry adder”**.


Here is an example of its output. The 4-bit sum is truncated to 1001.

$$\begin{array}{r} 1110 \\ +1011 \\ \hline 11001 \end{array}$$

Note that the unit's adder is implemented using a full adder.
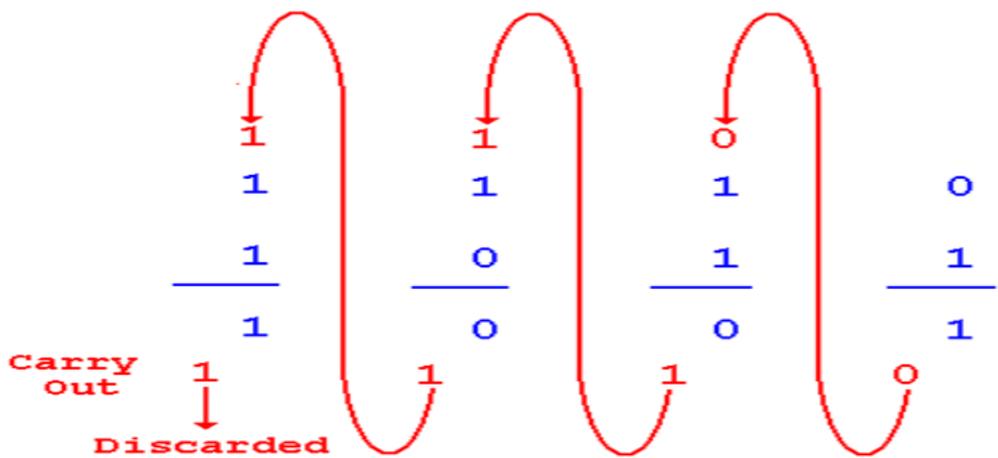
## Propagating the Carry Bits

Just as in standard arithmetic, when done by hand, the carry of one stage is propagated as a carry-in to the next higher stage.



## Addition and Subtraction

In order to convert a ripple-carry adder into a subtractor, we employ the standard algebra trick:  $A - B$  is the same as  $A + (-B)$ .

In order to subtract  $B$  from  $A$ , it is necessary to negate  $B$  to produce  $-B$ , and then to add that number to  $A$ .

We now have to develop a circuit that will negate a binary value.

In order to do this, we must stipulate the method used to represent signed integers. As in earlier lecture, we use **two's-complement** notation.

In this method, in order to negate a binary integer, it is necessary to produce the two's-complement of that value.

1. First, take the one's-complement of the binary integer, and then
2. Add 1 to that value.


We have to develop a circuit to create the one's-complement of a binary integer. We shall develop two circuits to do this.

### The One's Complement of a Binary Integer

In order to take the one's-complement of an integer in binary form, just change every 0 to a 1, and every 1 to a 0. Here are some examples.

Original value	<b>0110 0111</b>	<b>1010 0011</b>
One's complement	<b>1001 1000</b>	<b>0101 1100</b>

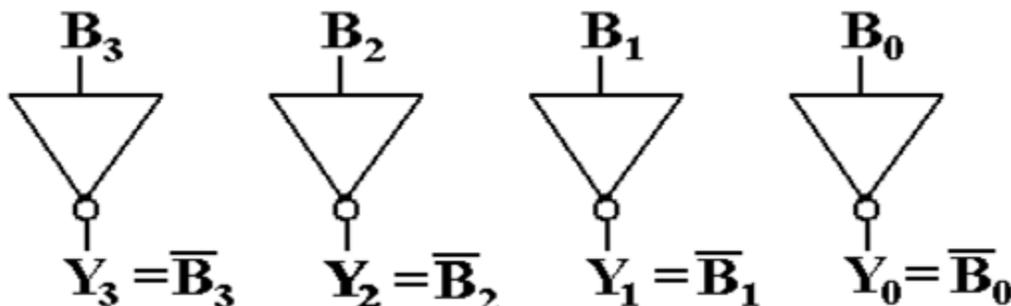The circuit that does this conversion is the NOT gate. The circuit below would be used for four-bit integers.




If the input is  $B_3B_2B_1B_0 = 0110$ , the output is  $Y_3Y_2Y_1Y_0 = 1001$ .

This circuit can be extended to any number of bits required.
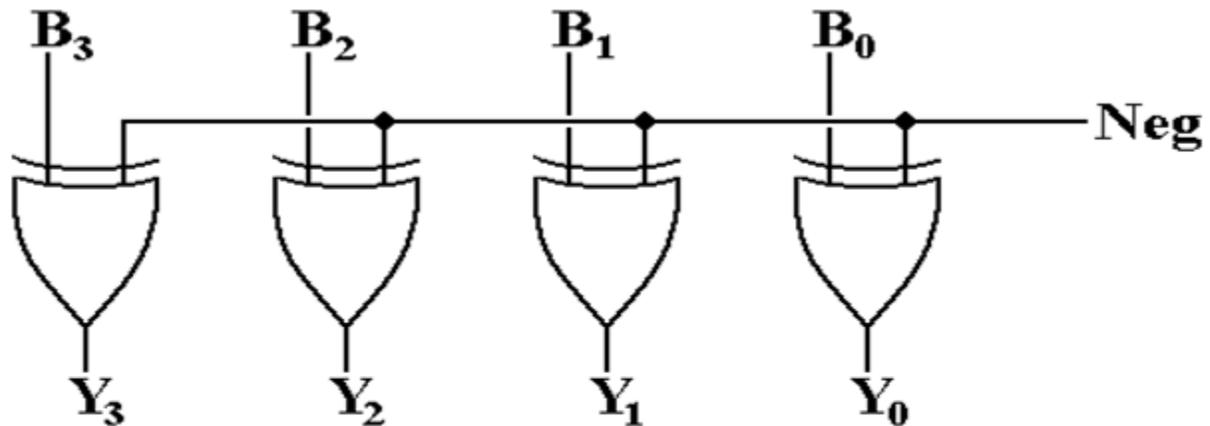
### The XOR Gate as a NOT Gate

In order to make an adder/subtractor, it is necessary to use a gate that can either pass the value through or generate its one's-complement.

The exclusive OR gate, XOR, is exactly what we need.



**If Neg = 0 Then  $Y_3 = B_3, Y_2 = B_2, Y_1 = B_1,$  and  $Y_0 = B_0$**

**If Neg = 1 Then  $Y_3 = \bar{B}_3, Y_2 = \bar{B}_2, Y_1 = \bar{B}_1,$  and  $Y_0 = \bar{B}_0$**

This is controlled by a single binary signal: Neg.

Let  $B = 1011$ . If  $Neg = 0$ , then  $Y = 1011$ . If  $Neg = 1$ , then  $Y = 0100$ .

### **Some Notation for Bit-Wise Operations**

Taking the one's-complement of a binary integer involves taking the one's-complement of each of its bits. We use the NOT notation to denote the one's-complement of the entire integer.

If  $B = B_3B_2B_1B_0$  is a four-bit binary number, its one's-complement is

$$\bar{B} = \bar{B}_3 \bar{B}_2 \bar{B}_1 \bar{B}_0$$

Remember that to get the two's-complement, one takes the one's-complement and adds one. In two's-complement arithmetic we have:  $\underline{-B = \bar{B} + 1}$ .


This suggests the use of an adder to produce the negative. For  $B = B_3B_2B_1B_0$ ,

we take the one's complement to start the negation process. The addition of 1, necessary to take the two's-complement, is achieved by setting the carry-in of the unit's full-adder to 1.

This is the reason for using a full-adder in the unit's position. We can alternate between an adder and subtractor. More on this a bit later.
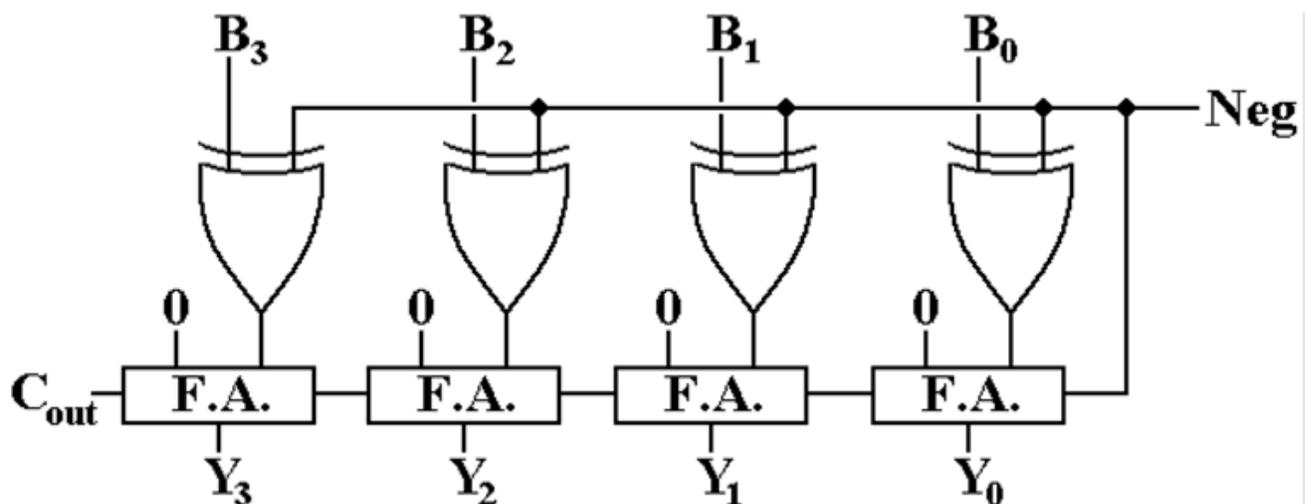
### The Negator Circuit

Here is the circuit to produce the negative of a 4-bit number  $B = B_3B_2B_1B_0$ .




If  $Neg = 0$ , then the XOR gates pass the values  $B_3B_2B_1B_0$  unchanged and the ripple-carry adder adds 0 to that. The result is  $Y = B$ .

If  $Neg = 1$ , then the XOR gates cause the one's-complement of  $B = B_3B_2B_1B_0$  to be computed. Note that the carry-in of the full adder is set to 1, so that it adds 1 to the one's-complement, thus producing the negative:  $Y = -B$ .
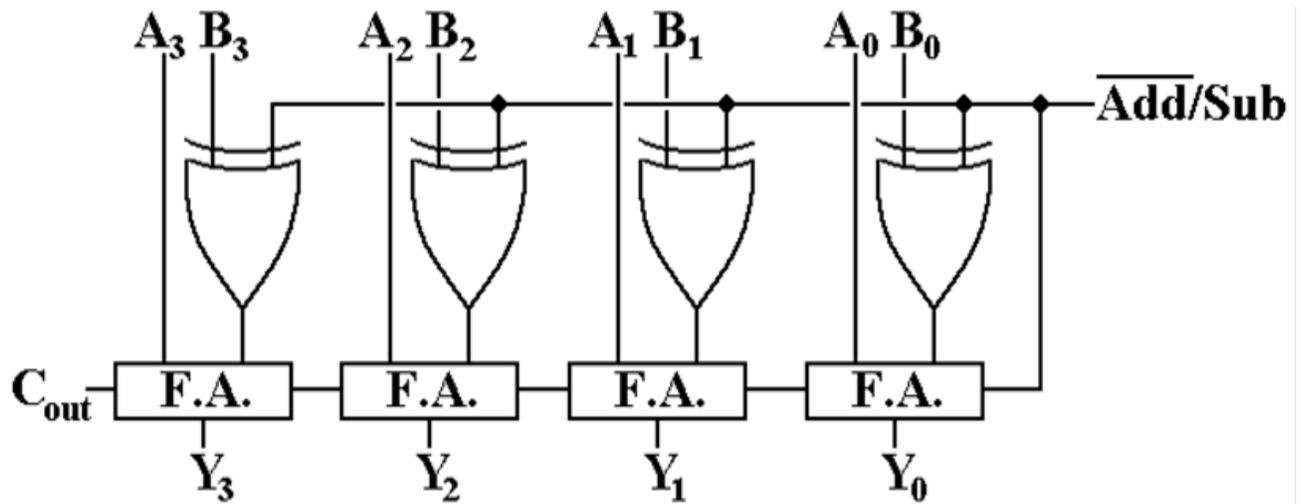
### The Full Adder/Subtractor

We now have the circuit that either adds or subtracts. This is a 4-bit circuit that produces either  $(A + B)$  or  $(A - B)$ .



### $\overline{\text{Add/Sub}}$

This notation is used for a two-valued control signal. When the value is 0, the circuit is to add, when it is 1 the circuit is to subtract.

This adder/subtractor can be extended to any number of binary bits.